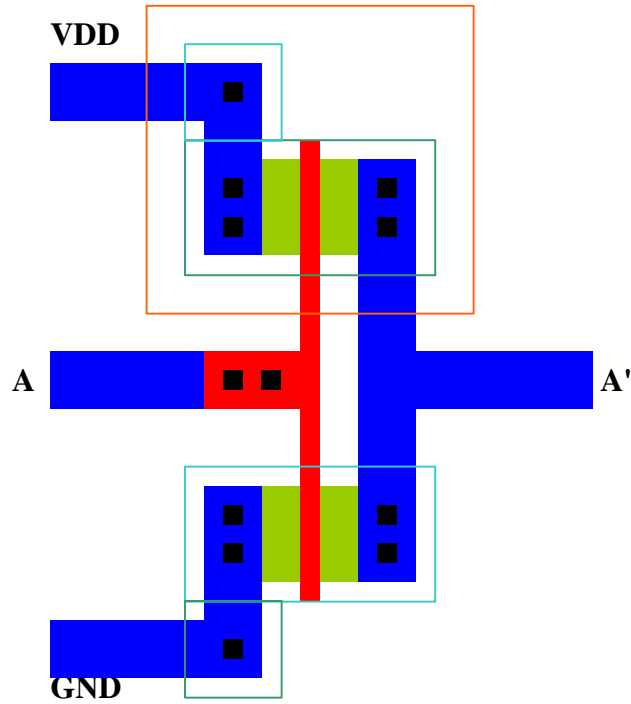


SIMPLE CMOS GATES

INVERTER



NAND GATE

