


LOW CARBON FOOTPRINT HYBRID BATTERY CHARGER

PROJECT PROGRESS




Students: Blake Kennedy, Phil Thomas
Advisors: Dr. Huggins, Mr. Gutschlag, Dr. Irwin
Date: March 3, 2008


PRESENTATION OUTLINE

- Project Status
 - Time Management
 - Project Delays
 - Updated Flowchart
 - Updated Materials
- Project Updates
 - Buck-Boost Scheme
 - Charger Scheme
 - PSPICE Simulations
 - Controller & Software Design

PROJECT STATUS


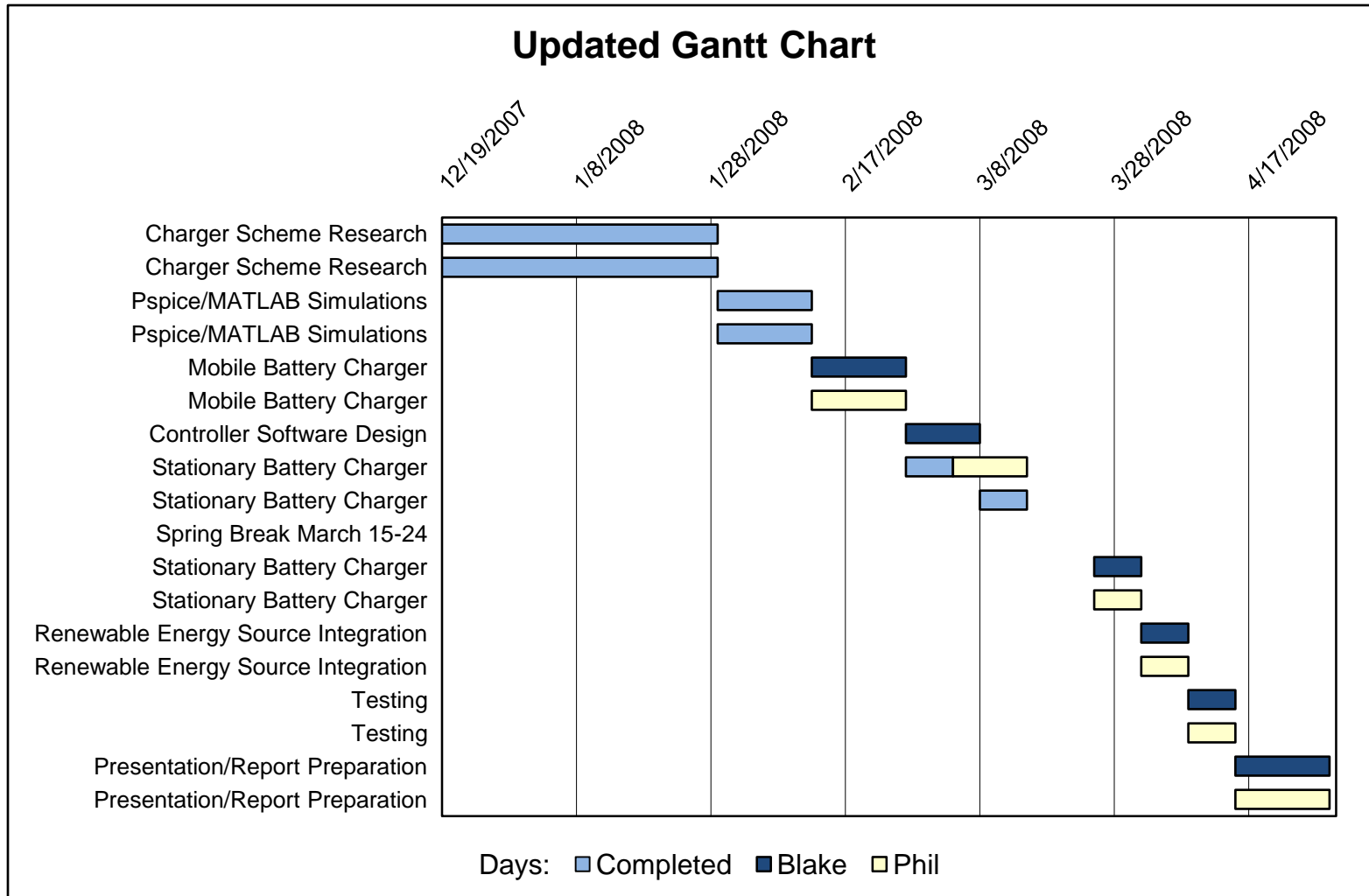


PROJECT STATUS

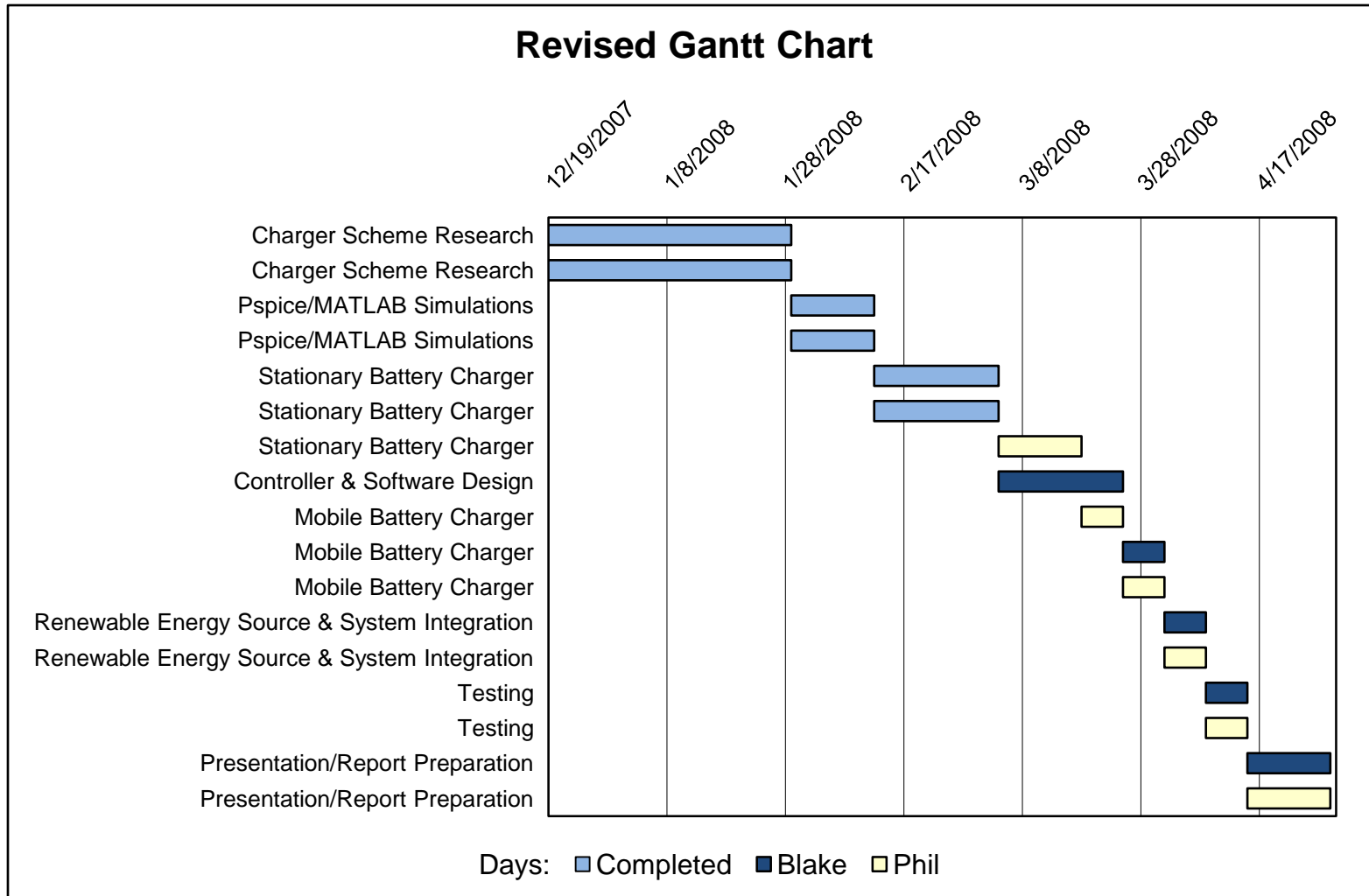


PROJECT DELAYS

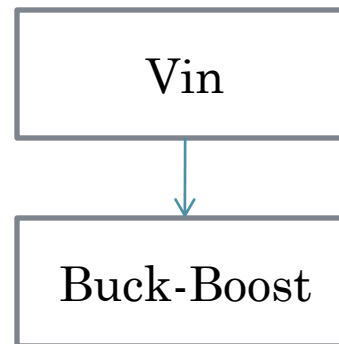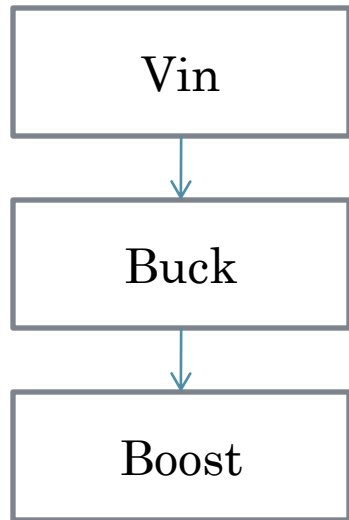- Research
 - Major Setback
 - More research than anticipated
 - Probably should have taken EE430 last year
 - One week research spent on Buck then Boost topologies
 - Scraped plans and used Buck-Boost topology
 - Less parts needed
 - Simply makes more sense for this application




PROJECT DELAYS

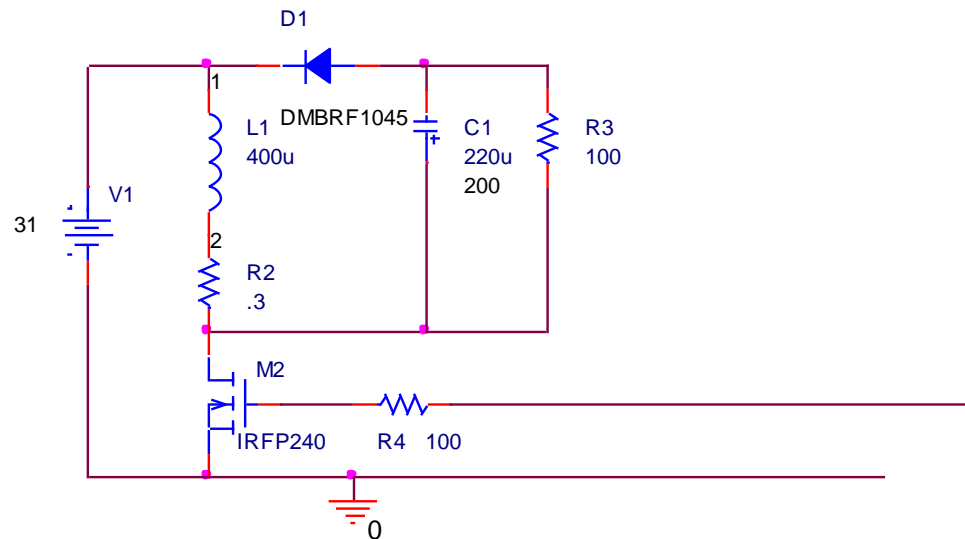- Simulations Round I
 - About one day spent troubleshooting PSPICE
 - MOSFET switching
 - Initially, planned use of a p channel MOSFET
 - Switched to n channel
 - Lower Rds-On Value
 - Utilize mutual ground with source
 - Simpler topology




PROJECT DELAYS

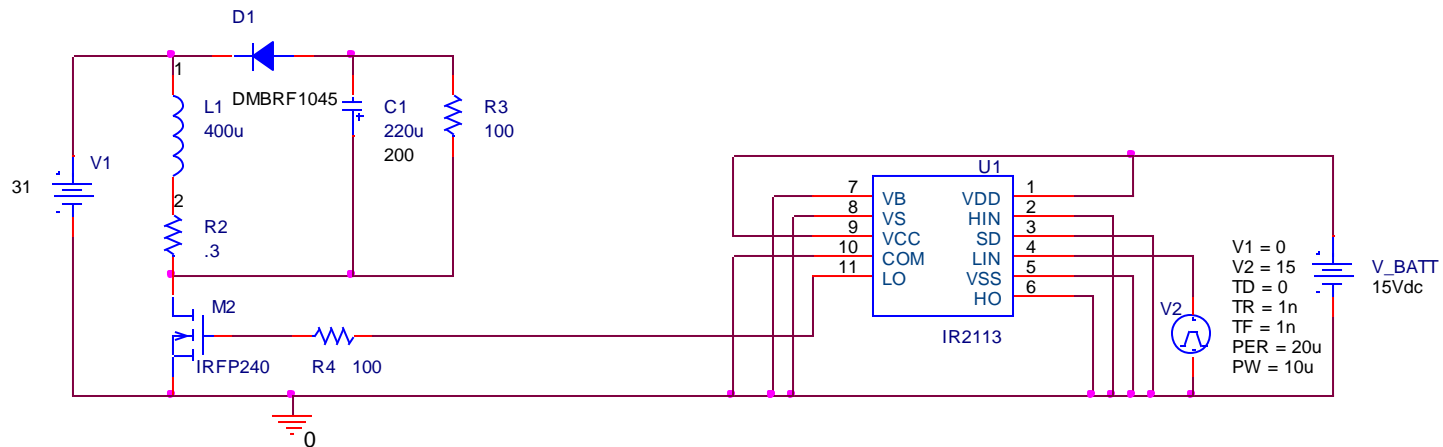
- Implementation Round I
 - MOSFET was stuck in linear mode
 - Gate driver needed
- Simulations Round II
 - Vout was stuck around 21 Volts for 40V input.
 - Vds was greater than maximum
 - Replaced MOSFET
 - Confirmed gate driver setup



OLD HIGH LEVEL FLOWCHART

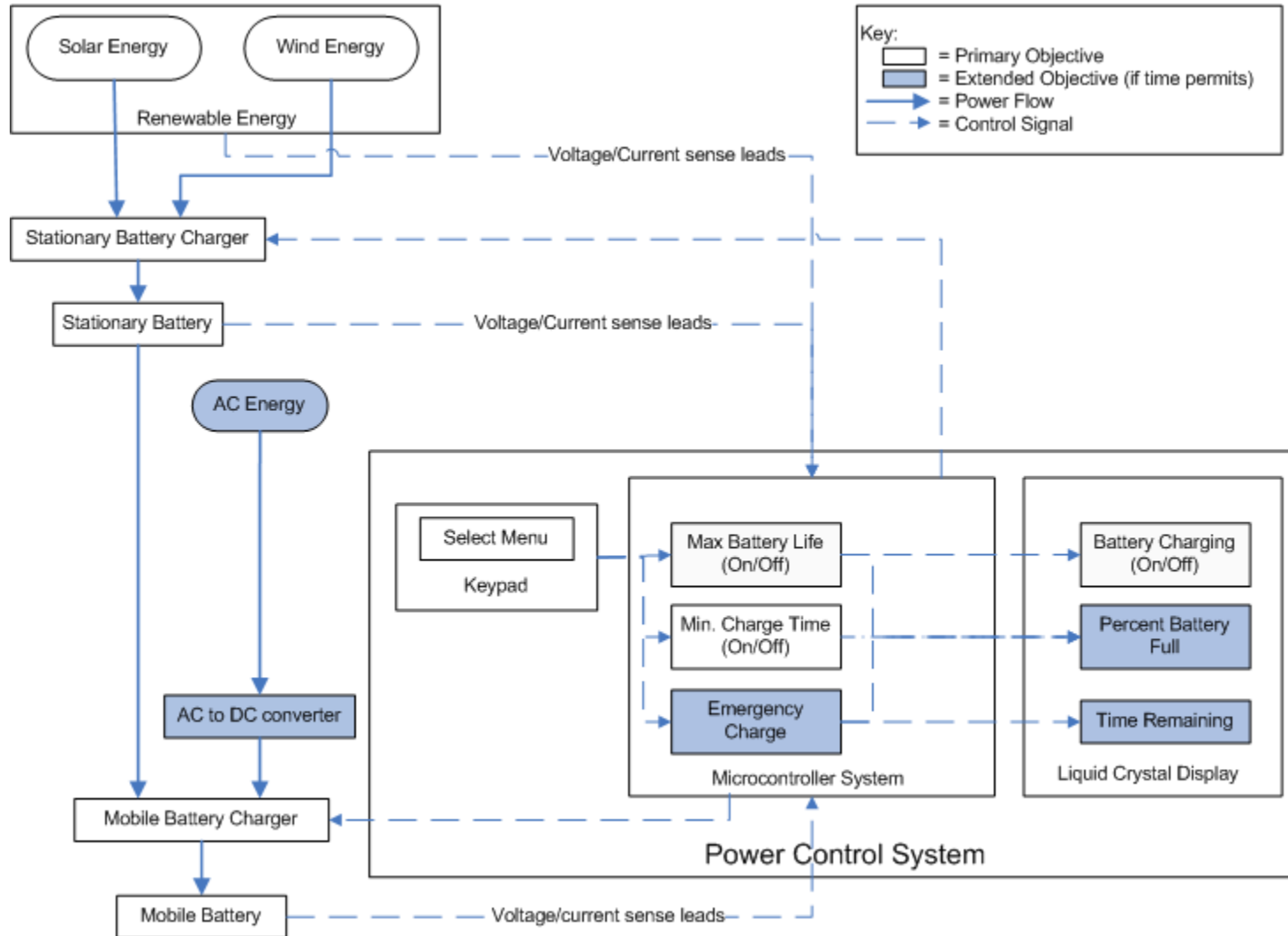

LOW LEVEL FLOWCHART

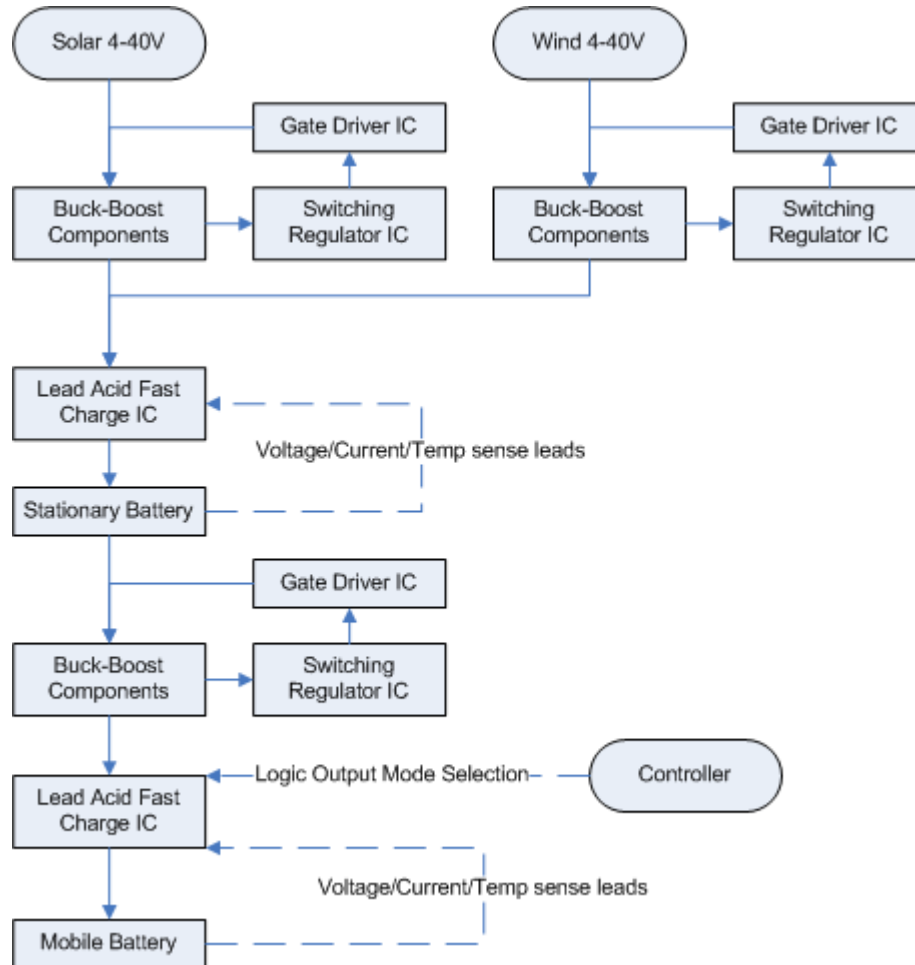

UPDATED MATERIALS

- Stationary Battery
- Optima D31T
 - Lead Acid
 - 75 Ah, 12V
 - Low cost
 - No Memory Effect



Battery Charger (Constant Voltage):	13.8 to 15.0 volts; 10 amps maximum; 6-12 hours approximate
Float Charge:	13.2 to 13.8 volts; 1 amp maximum (indefinite time at lower voltages)
Rapid Recharge: (Constant voltage charger)	Maximum voltage 15.6 volts. No current limit as long as battery temperature remains below 125°F (51.7°C). Charge until current drops below 1 amp.

UPDATED MATERIALS

- Photovoltaic (P.V.) Array
 - Had planned to use Kyocera KC50T
 - Using BP 350J
 - 50W, 17.5V, 2.9A at max power



UPDATED MATERIALS

- BP 350J Efficiency
- 72 modules (0.042m x 0.125m)
- Solar Panel Area = 0.378m²
- Nominal Sun Power Density: 1kW/m²
- Maximum Panel Power: 0.050 kW
- Efficiency: $0.050\text{kW}/(0.378\text{m}^2 \cdot 1\text{kW}/\text{m}^2)$
= 13.22 %

ANALYTICAL CALCULATIONS

○ Load Calculation

- Capacity $12V \cdot 12Ah = 144Wh$
- $144 W \cdot 3,600 \text{ sec} \cdot 1.25 = 648,000 J$

○ Solar Power Calculation

- Efficiency * Area * Sun hours * 3,600 seconds
- Maximum Spec $50W = 180,000 J/\text{hour} / \text{panel}$
- Worst Case for Chicago = 206,449 J/day

○ Worst Case Number of Solar Modules


- $648,000 J / 285,768 J = 2.45 \text{ P.V. Modules}$




BUCK-BOOST SCHEME

- Buck-Boost Voltage Regulator Topology
- Energy Stored in Inductor
- Inductor supplies energy to load
- Capacitor supplies energy to load when in the “on-state”
- Will operate in continuous mode

On-State

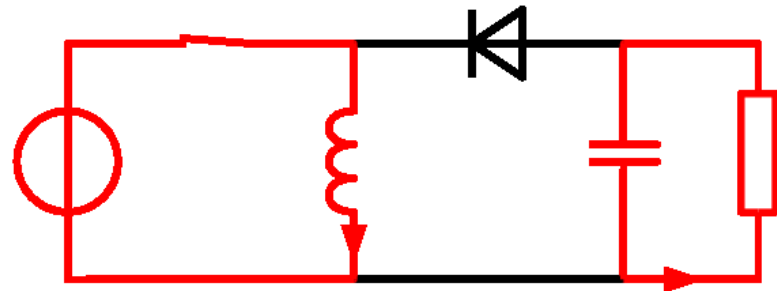


Off-State

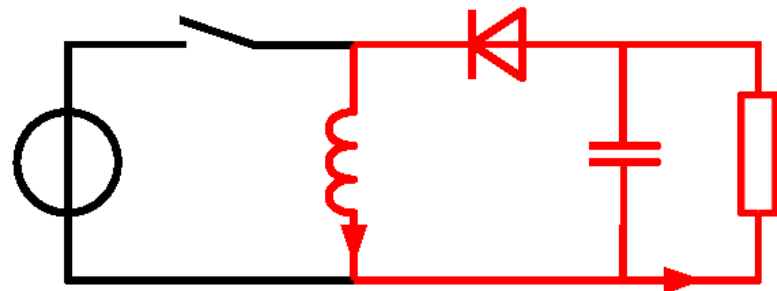

BUCK-BOOST SCHEME

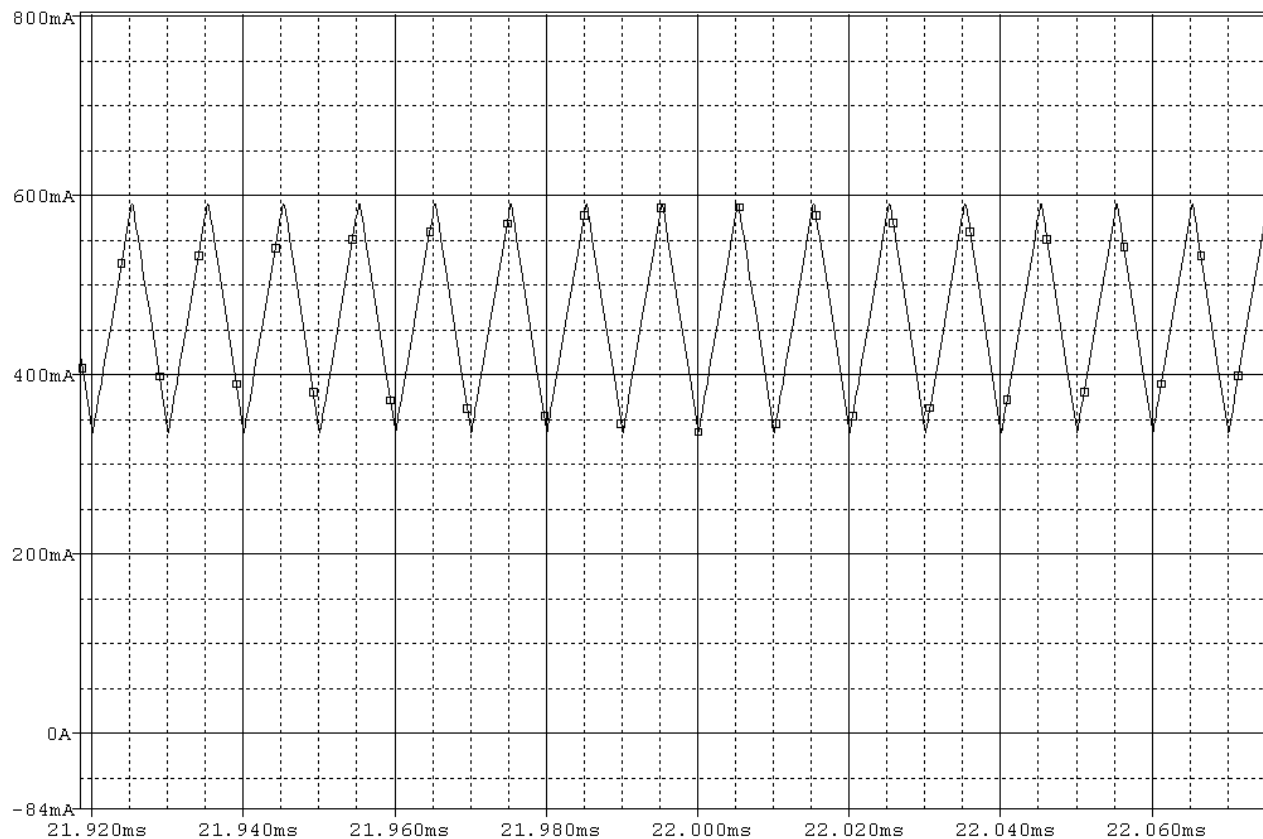- Buck-Boost Voltage Regulator Topology
- Continuous mode- Inductor Current




BUCK-BOOST SCHEME

○ Implementation Considerations

- Inductor energy must be large enough to store required energy
- Inductor must be large enough to be in continuous mode
- Switching speed must be fast enough to remain in continuous mode
- Capacitor must be large enough to supplement inductor when switch is closed
- Diode must have:
 - high reverse bias ratings
 - low voltage drop
 - fast recovery
- Inductor, FET, and Diode have high current


BUCK-BOOST IMPLEMENTATION

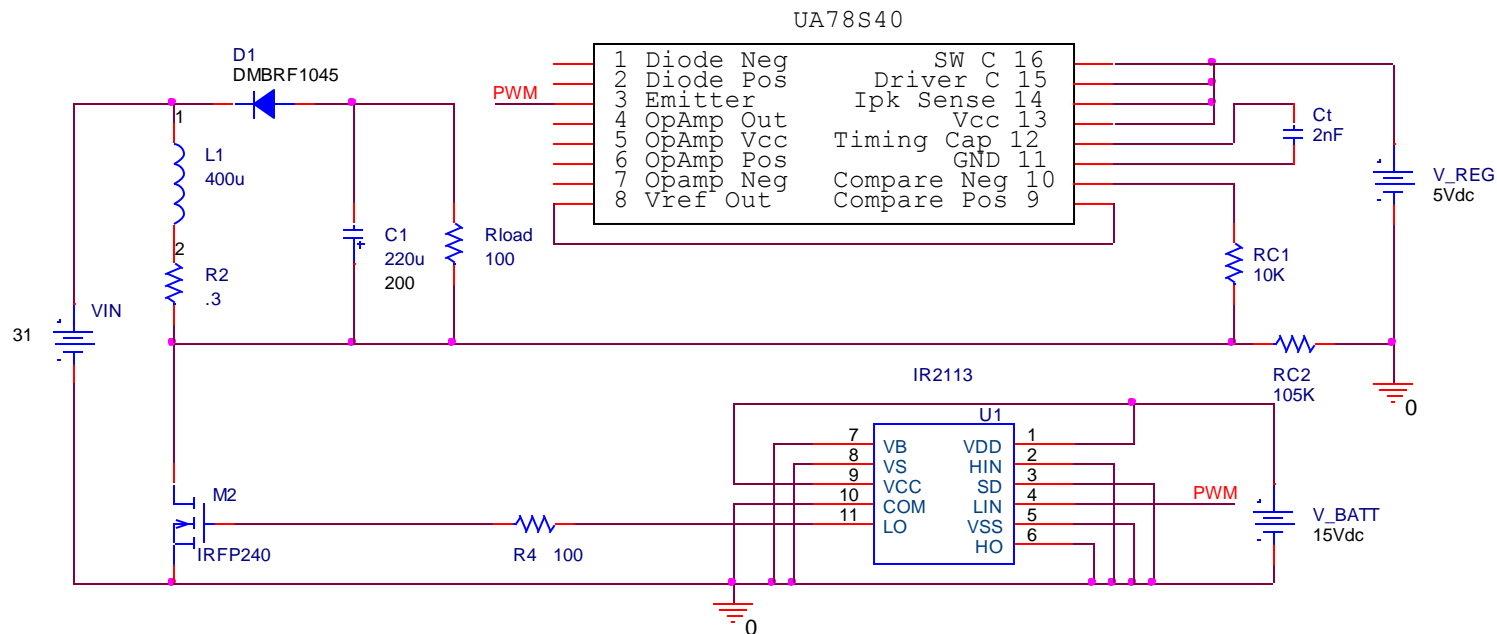- Values determined from maximum and minimum V_{in} voltage simulations only
- Next step is to theoretically figure minimum values for Inductor and Capacitor



BUCK-BOOST IMPLEMENTATION

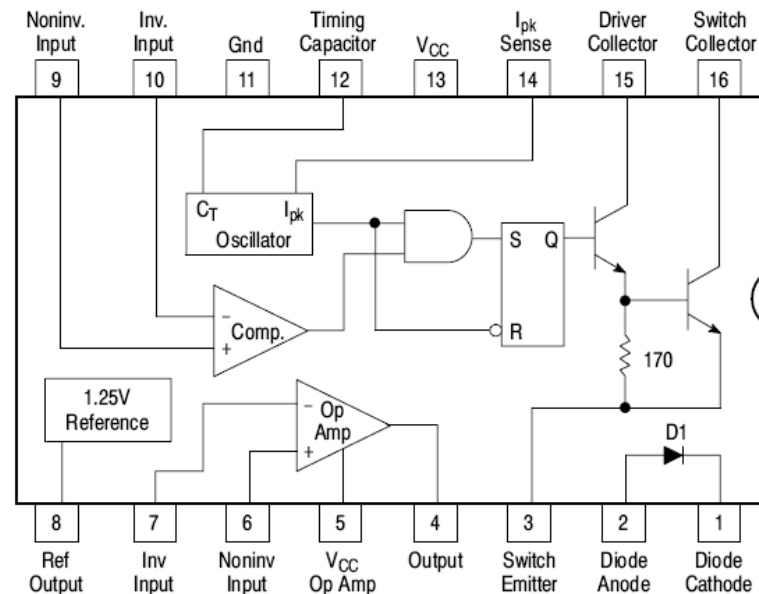
- UA78S40
- Universal Switching Regulator Subsystem
- Provides PWM Closed Loop Control
 - Scales down output voltage and compares to 1.25V
 - Voltage divider must have 1% resistor tolerance
 - Variable frequency range from 1Khz – 100Khz
 - Faster switching allows for lower inductance
 - Eliminates need for developing a stable control system in software
 - 0-40V PWM output
 - Vcc= 5V used



BUCK-BOOST IMPLEMENTATION


- IR2113
- High and Low Side Driver
- Ability to operate at 100KHz
- Separate logic supply range from 3.3V to 20V
- $LO = V_{dd} = V_{batt} = 12-13.5V$

Typical Connection

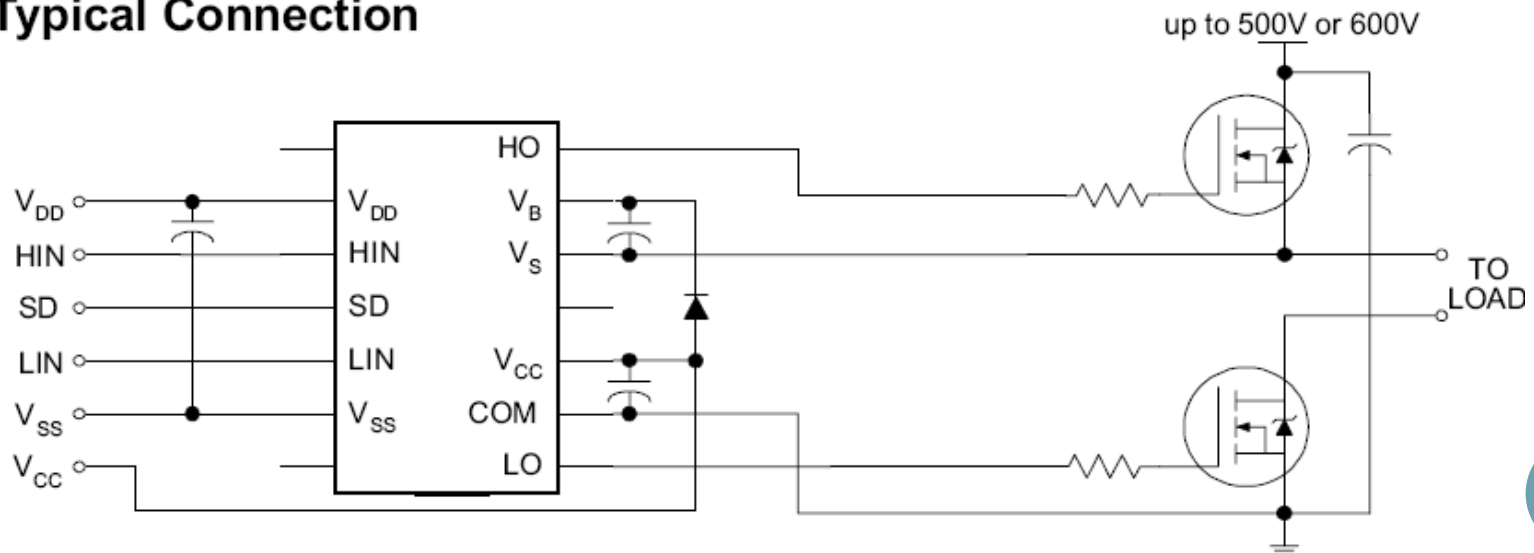

BUCK-BOOST IMPLEMENTATION

○ IR2113

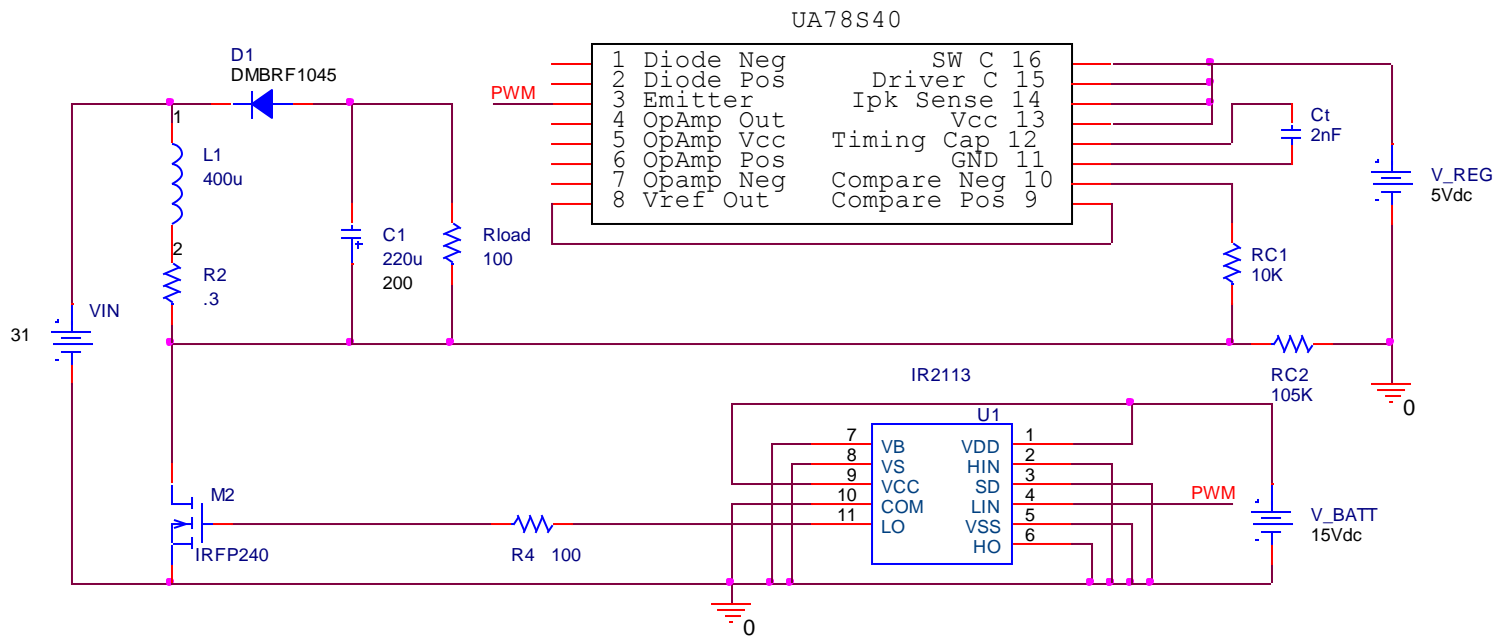


STATIONARY CHARGER SCHEME

- BQ2031
- Lead Acid Fast Charge IC
- Two-Step Voltage Control
 - Automatically detects low current and switches to trickle charge
 - Temperature-compensated
 - PWM Control of output
 - Automatically detects shorted, opened, or damaged cells

STATIONARY CHARGER SCHEME


- BQ2031
- Lead Acid Fast Charge IC

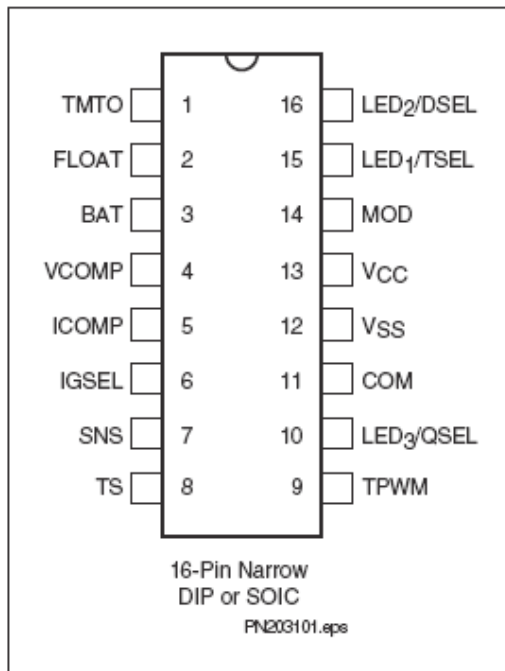

TMTO	Time-out timebase input	LED ₃ / QSEL	Charge status output 3/ Charge algorithm select input 1
FLOAT	State control output	COM	Common LED output
BAT	Battery voltage input	V _{SS}	System ground
VCOMP	Voltage loop comp input	V _{CC}	5.0V±10% power
ICOMP	Current loop comp input	MOD	Modulation control output
IGSEL	Current gain select input	LED ₁ / TSEL	Charge status output 1/ Charge algorithm select input 2
SNS	Sense resistor input	LED ₂ / DSEL	Charge status output 2/ Display select input
TS	Temperature sense input		
TPWM	Regulator timebase input		

STATIONARY CHARGER SCHEME

- BQ2031
- Two-Step Voltage Charge

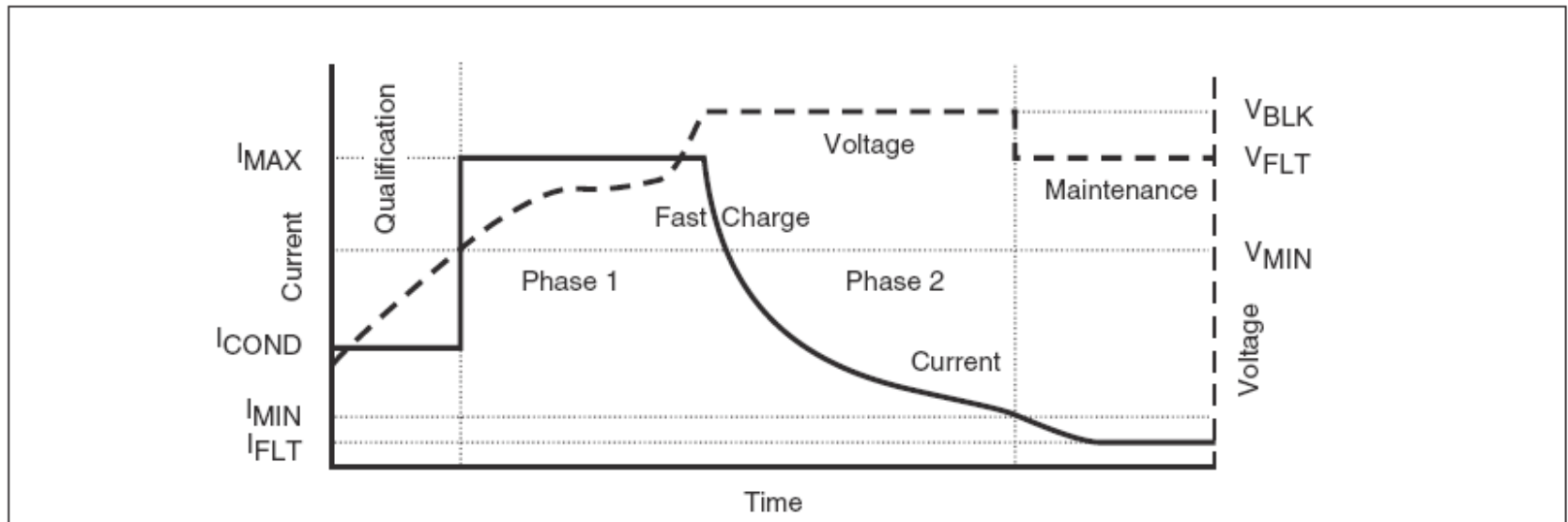

STATIONARY CHARGER SCHEME

- BQ2031
- Configuring Charging Algorithm

Algorithm/State	QSEL	TSEL	Conditions	MOD Output
Two-Step Voltage	L	H/L ^{Note 1}	-	-
Fast charge, phase 1			while $V_{BAT} < V_{BLK}$, $I_{SNS} = I_{MAX}$	Current regulation
Fast charge, phase 2			while $I_{SNS} > I_{MIN}$, $V_{BAT} = V_{BLK}$	Voltage regulation
Primary termination			$I_{SNS} = I_{MIN}$	
Maintenance			$V_{BAT} = V_{FLT}$	Voltage regulation
Two-Step Current	H	L	-	-
Fast charge			while $V_{BAT} < V_{BLK}$, $I_{SNS} = I_{MAX}$	Current regulation
Primary termination			$V_{BAT} = V_{BLK}$ or $\Delta^2V < -8mV$ ^{Note 2}	
Maintenance			I_{SNS} pulsed to average I_{FLT}	Fixed pulse current
Pulsed Current	H	H	-	-
Fast charge			while $V_{BAT} < V_{BLK}$, $I_{SNS} = I_{MAX}$	Current regulation
Primary termination			$V_{BAT} = V_{BLK}$	
Maintenance			$I_{SNS} = I_{MAX}$ after $V_{BAT} = V_{FLT}$; $I_{SNS} = 0$ after $V_{BAT} = V_{BLK}$	Hysteretic pulsed current

STATIONARY CHARGER SCHEME

○ BQ2031

○ Voltage and Current Monitoring

The resistor values are calculated from the following:

Equation 1

$$\frac{RB1}{RB2} = \frac{(N * V_{FLT})}{2.2V} - 1$$

Equation 2


$$\frac{RB1}{RB2} + \frac{RB1}{RB3} = \left(\frac{N * V_{BLK}}{2.2}\right) - 1$$

Equation 3

$$I_{MAX} = \frac{0.250V}{R_{SNS}}$$

where:

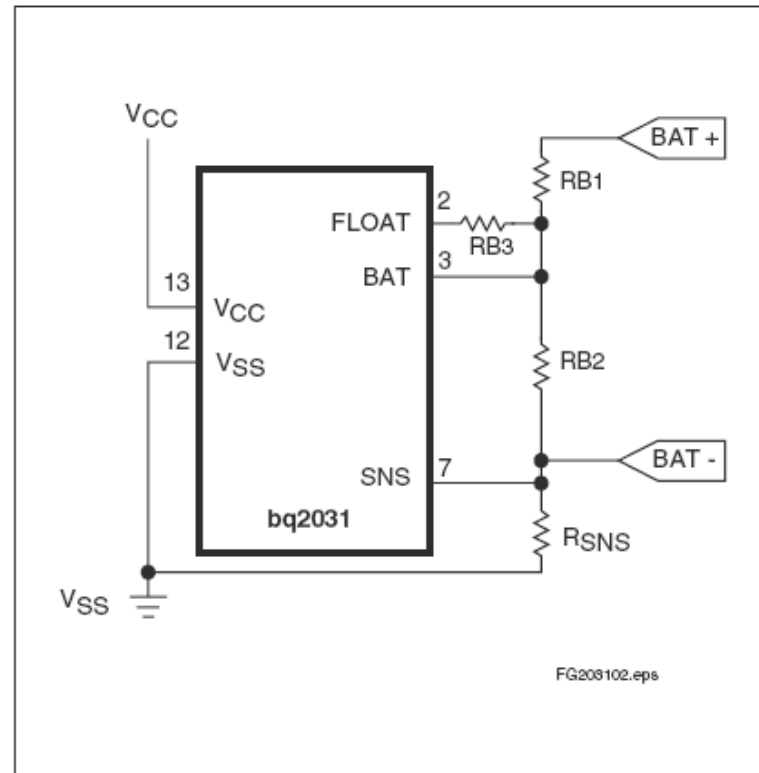- N = Number of cells
- V_{FLT} = Desired float voltage
- V_{BLK} = Desired bulk charging voltage
- I_{MAX} = Desired maximum charge current



STATIONARY CHARGER SCHEME

- BQ2031
- Voltage and Current Monitoring

- N=6 cells
- V_{flt}=13.3V
- V_{blk}=14.0V
- I_{max}=10A

- Using Equations
- R_{B1}=130KΩ
- R_{B2}=50KΩ
- R_{B3}=620KΩ

The resistor values are calculated from the following:

Equation 1

$$\frac{R_{B1}}{R_{B2}} = \frac{(N * V_{FLT})}{2.2V} - 1$$

Equation 2

$$\frac{R_{B1}}{R_{B2}} + \frac{R_{B1}}{R_{B3}} = \left(\frac{N * V_{BLK}}{2.2}\right) - 1$$

Equation 3

$$I_{MAX} = \frac{0.250V}{R_{SNS}}$$

where:

- N = Number of cells
- V_{FLT} = Desired float voltage
- V_{BLK} = Desired bulk charging voltage
- I_{MAX} = Desired maximum charge current

STATIONARY CHARGER SCHEME

- BQ2031
- Fast Charge cutoff to Trickle Charge
- IGSEL = 0
- $I_{min} = I_{max}/10 = 10A/10 = 1A$

IGSEL	I_{MIN}
0	$I_{MAX}/10$
1	$I_{MAX}/20$
Z	$I_{MAX}/30$

STATIONARY CHARGER SCHEME

- BQ2031
- Temperature Sensing
- Thermistors have been ordered but calculations have not been done yet.

Equation 4

$$0.6 * V_{CC} = \frac{(V_{CC} - 0.250V)}{1 + \frac{RT1 * (RT2 + R_{LTF})}{(RT2 * R_{LTF})}}$$


Equation 5

$$0.44 = \frac{1}{1 + \frac{RT1 * (RT2 + R_{HTF})}{(RT2 * R_{HTF})}}$$

where:

- R_{LTF} = thermistor resistance at LTF
- R_{HTF} = thermistor resistance at HTF

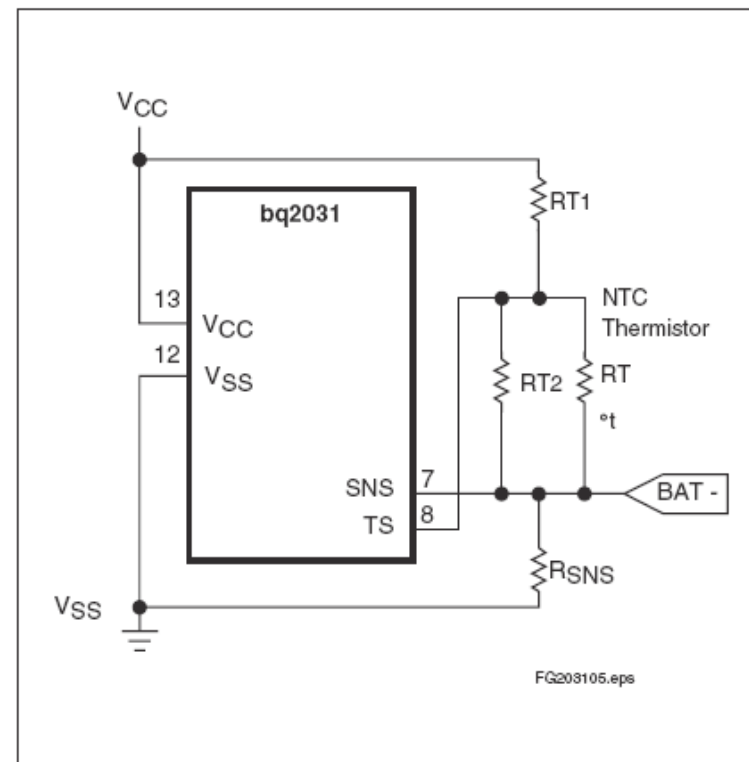TCO is determined by the values of RT1 and RT2. 1% resistors are recommended.




STATIONARY CHARGER SCHEME

- BQ2031
- Setting Charging Maximum Timeout
- $t_{mto}=24\text{hours}$
- $R=24\text{hrs}/(.5*.1\mu\text{F})$
- $= 480\text{G}\Omega$
- Use largest resistance possible or open circuit

Equation 6

$$t_{MTO} = 0.5 * R * C$$

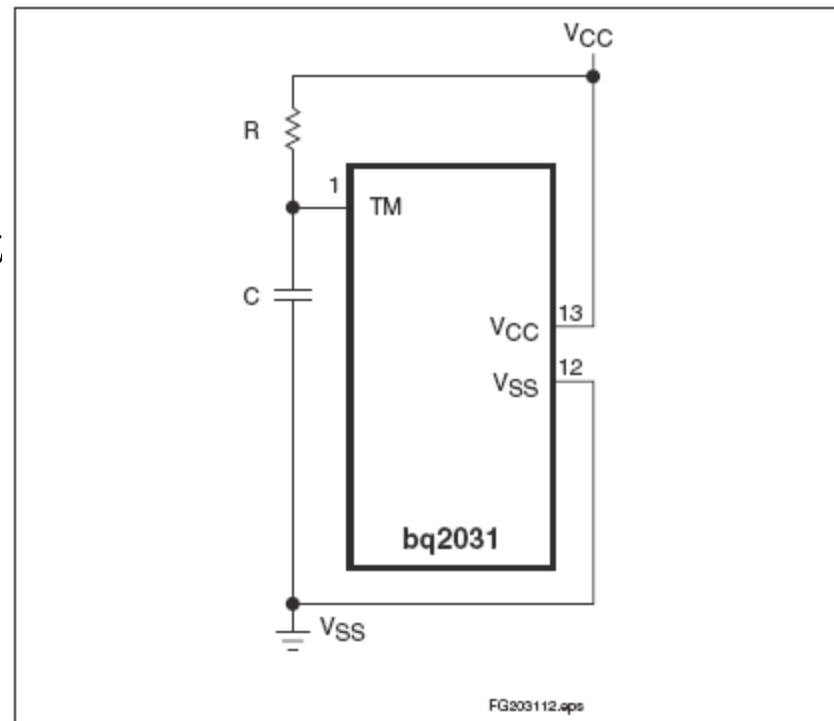where R is in $\text{k}\Omega$, C is in μF , and t_{MTO} is in hours. Typically, the maximum value for C of $0.1\mu\text{F}$ is used.



STATIONARY CHARGER SCHEME

- BQ2031
- Set switching frequency
- $F_{pwm}=100\text{KHz}$

Equation 9

$$F_{PWM} = 0.1/C_{PWM}$$

where C is in μF and F is in kHz. A typical switching rate is 100kHz, implying $C_{PWM} = 0.001\mu\text{F}$. MOD pulse width is modulated between 0 and 80% of the switching period.

STATIONARY CHARGER SCHEME


- BQ2031
- Voltage Loop stability
- Additional 17 page PDF explaining stability
- Adds external components to the IC
- Equations needed have been identified but will not be shown due to complexity and length
- We still need to determine exact values

STATIONARY CHARGER SCHEME

- The same buck-boost process and fast charge IC will be used except with different values
- The same design process will be used
 - Have not started yet
- Will have 2 modes of operation
 - Fast Charge & Trickle
 - Modes switched via microcontroller digital output


PSPICE SIMULATIONS- BUCK BOOST

- Minimum Input 6V with a 75% Duty Cycle

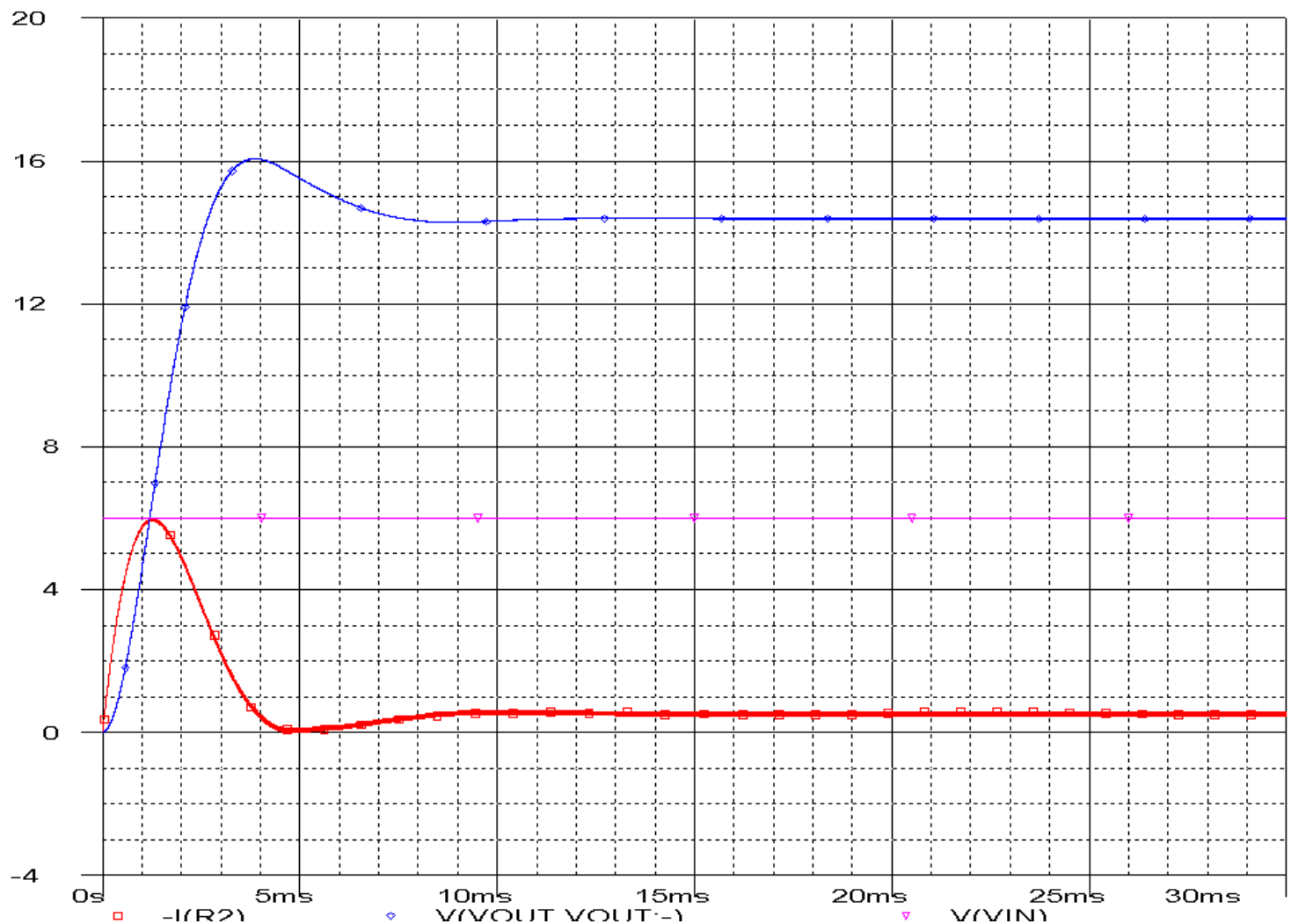


PSPICE SIMULATIONS- BUCK BOOST

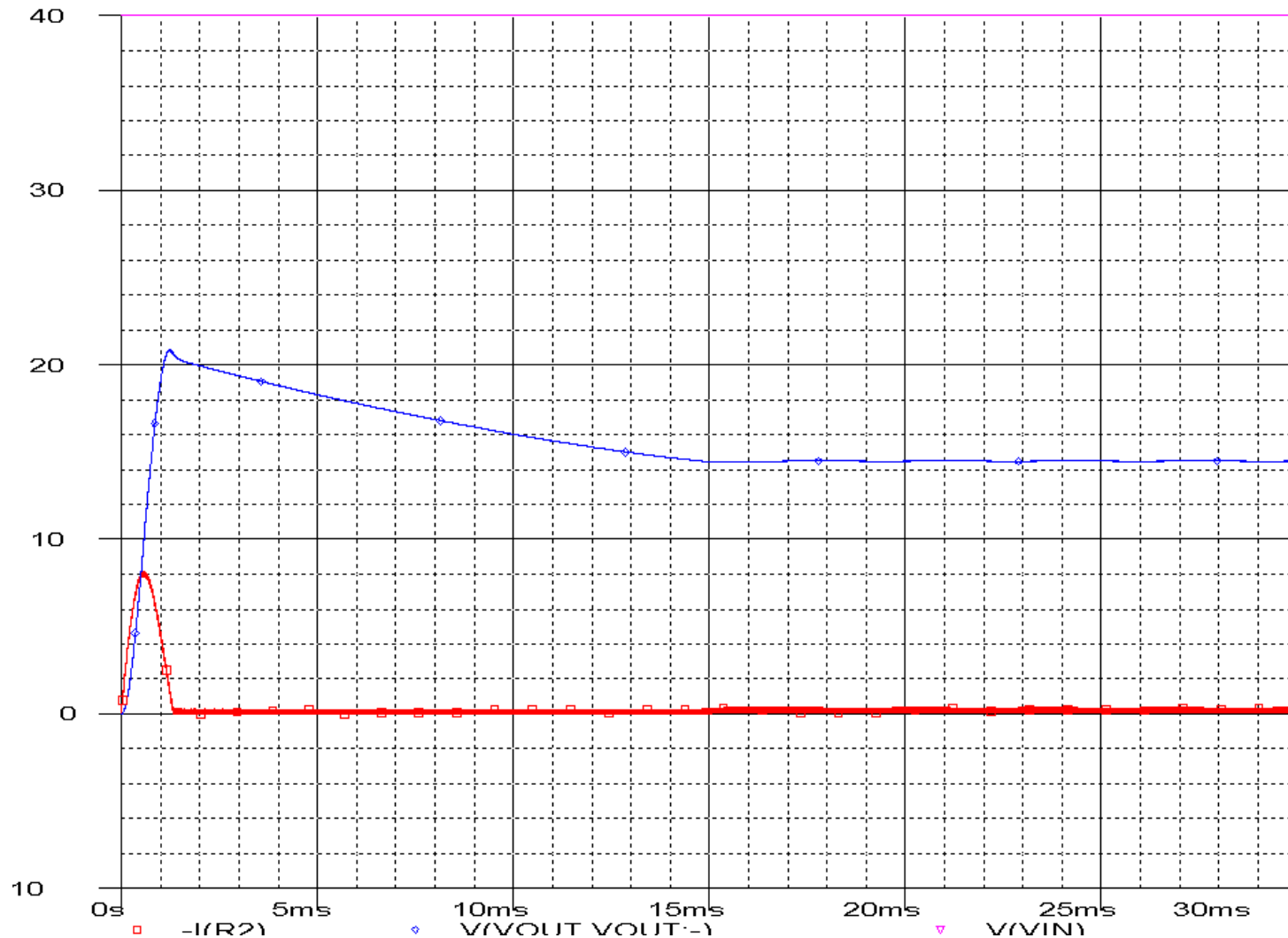- Maximum Input 40V with a 25% Duty Cycle




PSPICE SIMULATIONS- BUCK BOOST

- Input 20V with a 50% Duty Cycle

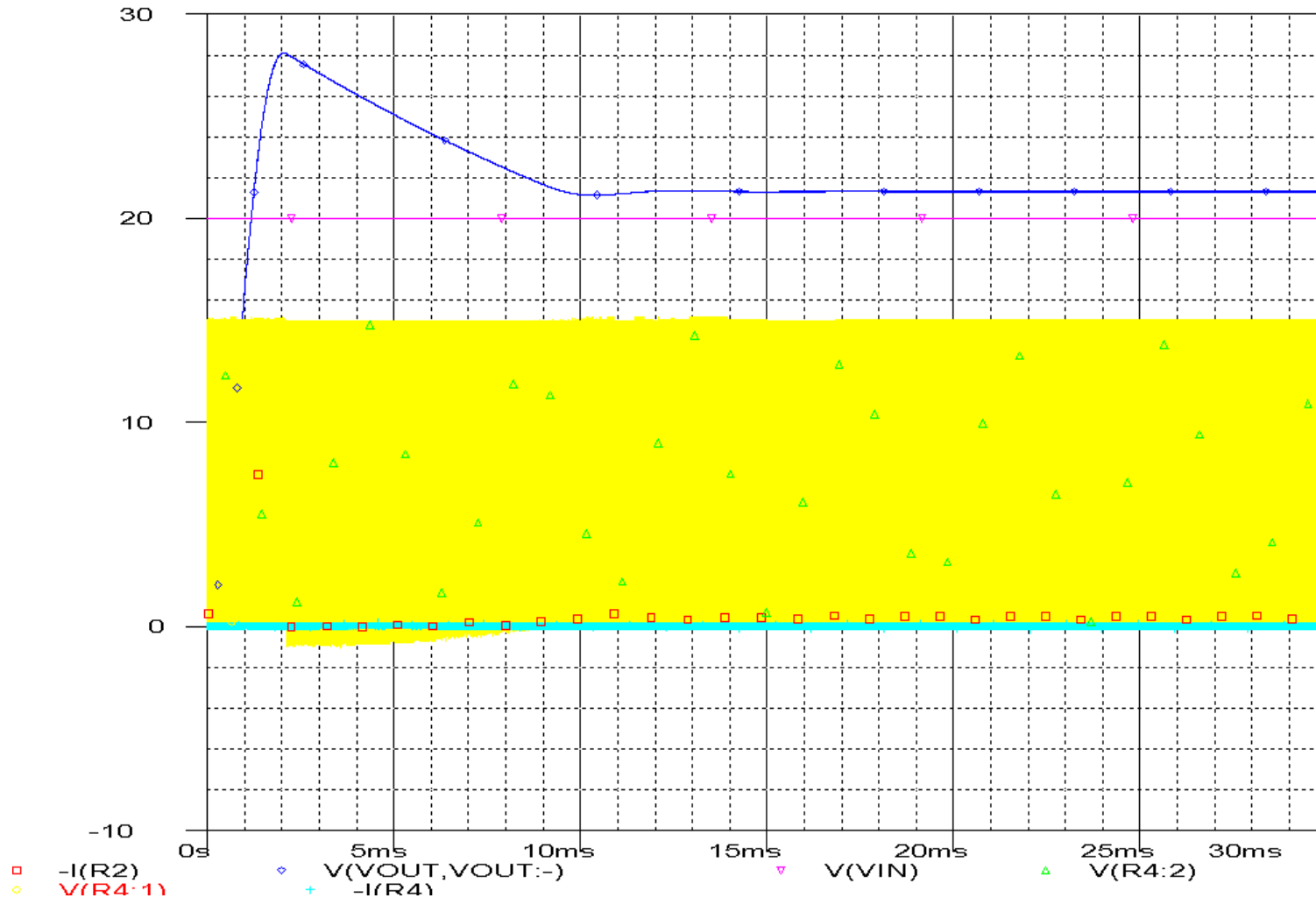

PSPICE SIMULATIONS- BUCK BOOST

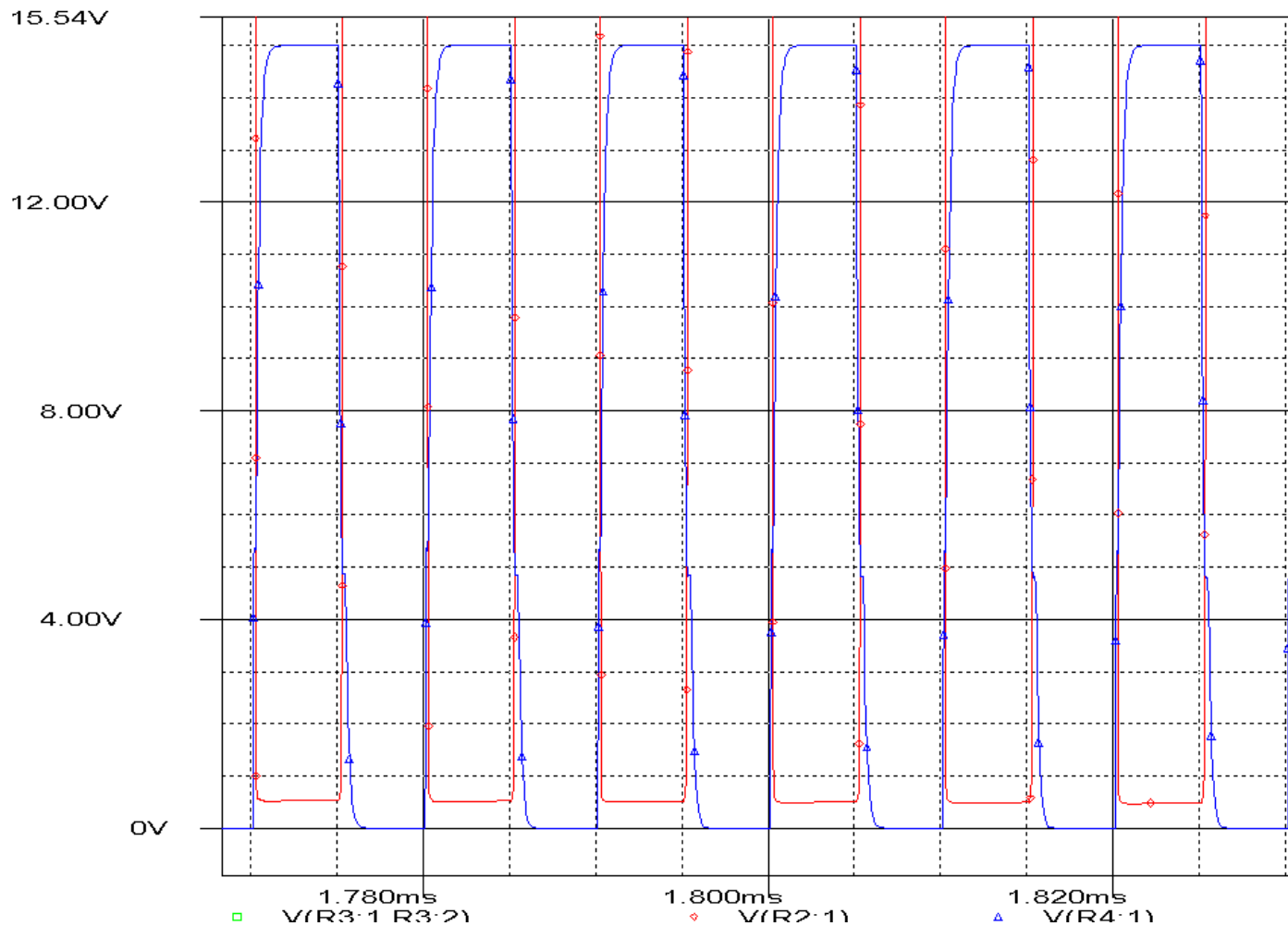- Switch Rate of 100KHz supported by IC model



CONTROLLER & SOFTWARE DESIGN

- Microcontroller switches IC charging mode
 - Feedback loop handled by IC
- Microcontroller Requirements
 - Keypad user input
 - 1 port needed
 - LCD user output
 - 1 port needed
 - Port pin IC input
 - 3 pins needed for status
 - Port pin IC output
 - 1 pin needed for switching modes

QUESTIONS?

